



**Experiment No. 3**

**Title: Design of digital system using Multiplexer.**



Batch: A2 Roll No.: 16010421063

Experiment No.: 3

**Aim:** Design of digital system using a Multiplexer**Resources needed:** Circuitverse online simulator or Hardware kit**Theory:**

Multiplexer also called Data selector. A digital circuit which selects one of the  $2^n$  data inputs and route it to the single output. Select lines are (n) and Input lines are ( $2^n$ )

 
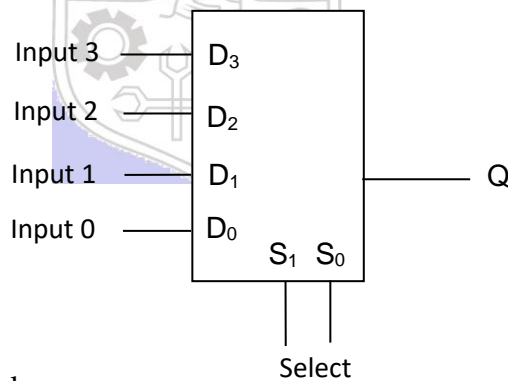


fig 1. A 2 : 1 multiplexer

In this case there are two input terminals  $D_0$  and  $D_1$ , one select input  $S_0$  and one output  $Q$ . When the select input is set to logic 0,  $D_0$  is connected to the output. When the select input is set to logic 1,  $D_1$  is connected to the output  $Q$ .

**Fig 2.** A 4 : 1 multiplexer.

In this case there are four data input terminals  $D_0 - D_3$ , two select inputs  $S_0$  and  $S_1$  and just one output  $Q$ . The following truth table shows when each of the data inputs is connected to the output.

| Select Inputs |       | Output |
|---------------|-------|--------|
| $S_1$         | $S_0$ | $Q$    |
| 0             | 0     | $D_0$  |
| 0             | 1     | $D_1$  |
| 1             | 0     | $D_2$  |
| 1             | 1     | $D_3$  |

**Table1.** Truth table for 4:1 multiplexer

 


fig 3. An 8 : 1 multiplexer.



| Select Inputs  |                |                | Output |
|----------------|----------------|----------------|--------|
| S <sub>2</sub> | S <sub>1</sub> | S <sub>0</sub> | Q      |
| 0              | 0              | 0              | D0     |
| 0              | 0              | 1              | D1     |
| 0              | 1              | 0              | D2     |
| 0              | 1              | 1              | D3     |
| 1              | 0              | 0              | D4     |
| 1              | 0              | 1              | D5     |
| 1              | 1              | 0              | D6     |
| 1              | 1              | 1              | D7     |

**Table2.** Truth Table for 8:1 Multiplexer



- The above truth table shows when the data inputs are connected to the output.
- Multiplexers are commonly used in communication systems; however they can be used in Logic System design and simplification as well.

**Exercise 1:** Show how an 8:1 multiplexer can be used to implement the logic function given below:-

$$F(A, B, C) = \sum m(0, 2, 5, 6, 7)$$

  

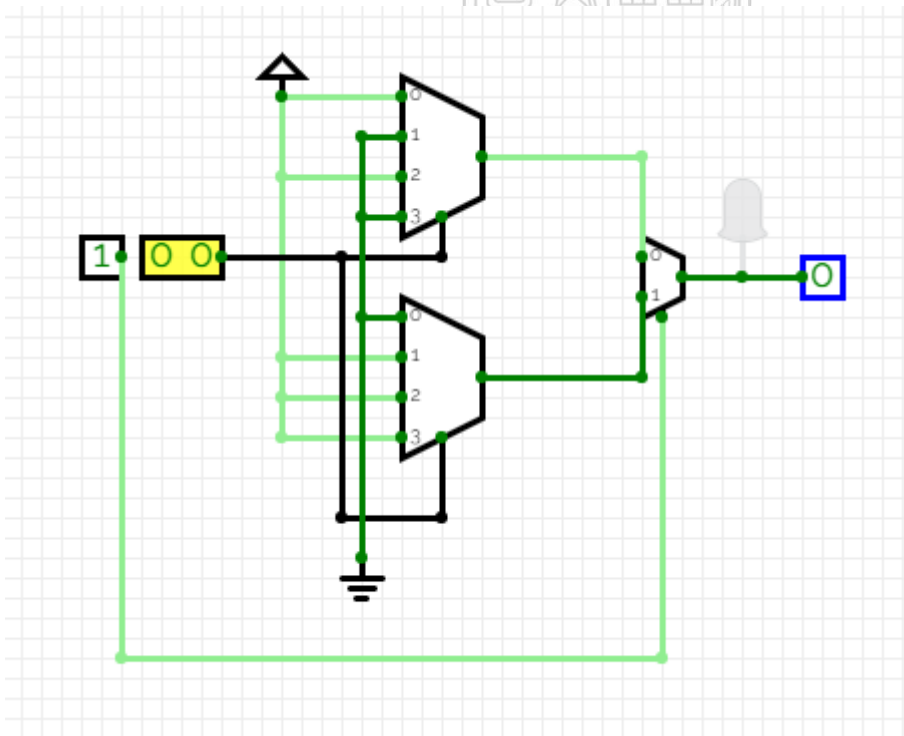 **Exercise 2:** Solve the above problem using two 4:1 multiplexers.




---

**Procedure:**

- Design logic circuits for given examples.

- b) Simulate / Connect the circuit for both cases and verify the outputs.
- c) Upload the write-up with the solved design problems given in write-up.

---

**Observations and Results:** Solve the examples as given in write-up/given during Lab session and Simulate as per instructions in Lab session

---

**Outcomes:**

**CO 2:** Understand the basic building blocks, techniques used in digital logic design.

**CO 3:** Design the combinational and sequential circuits using basic building blocks.

---

**Conclusion:**

An 8:1 multiplexer consists of eight data inputs D0 through D7, three input select lines S0 through S2 and a single output line Y. Depending on the select lines combinations, multiplexer selects the inputs.

Using the above concept we did a virtual representation of an 8:1 multiplexer. Similarly we converted an 8:1 to 4:1 using 2 4:1 multiplexers and 1 2:1 multiplexer and got the result. And printed the outcomes above.



**Grade: AA / AB / BB / BC / CC / CD /DD**

**Signature of faculty in-charge with date**

---

**References:**

**Books/ Journals/ Websites:**

1. R. P. Jain, "Modern Digital Electronics", Tata McGraw Hill.