

Batch: A2 Roll No.: 16010421063 Experiment No.: 4


Aim: Design a 4 bit binary to BCD convertor using the Circuitverse simulator.

Resources needed: Circuitverse online simulator

Theory:

- Although the CPU uses binary arithmetic for computation, the result has to be converted into decimal for display purpose. The token counter displays, railway platform displays, even calculator displays are all decimal displays. Conversion from binary to decimal is a non-trivial process. To reduce the processing overhead, BCD format offers a nice alternative
- In BCD (Binary Coded Decimal) format the decimal digits are stored as separate binary numbers. When these numbers are incremented, decremented or reset, only part of the remaining number needs to be changed. Also, the conversion from binary to decimal and unpacking of the digits is avoided.
- Because the BCD numbers are essentially decimal numbers, only 0-9 digits are used. Therefore when we do binary to BCD mapping, we either wrap around the numbers from 10 to 15 or we treat them as don't cares.

| Binary Code | Decimal | В | BCD Code | | | |
|-------------|---------|----------------|----------|---|----------------|----------------|
| ABCD | Number | B ₅ | B_4 | B | B ₂ | B ₁ |
| 0000 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0001 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0010 | 2 | 0 | 0 | 0 | 1 | 0 |
| 0011 | 3 | 0 | 0 | 0 | 1 | 1 |
| 0100 | 4 | 0 | 0 | 1 | 0 | 0 |
| 0101 | 5 | 0 | 0 | 1 | 0 | 1 |
| 0110 | 6 | 0 | 0 | 1 | 1 | 0 |
| 0111 | 7 | 0 | 0 | 1 | 1 | 1 |
| 1000 | 8 | 0 | 1 | 0 | 0 | 0 |
| 1001 | 9 | 0 | 1 | 0 | 0 | 1 |
| 1010 | 10 | 1 | 0 | 0 | 0 | 0 |
| 1011 | 11 | 1 | 0 | 0 | 0 | 1 |
| 1100 | 12 | 1 | 0 | 0 | 1 | 0 |
| 1101 | 13 | 1 | 0 | 0 | 1 | 1 |
| 1110 | 14 | 1 | 0 | 1 | 0 | 0 |
| 1111 | 15 | 1 | 0 | 1 | 0 | 1 |

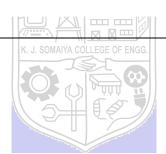


Procedure:

- a) Design logic circuit for the binary to BCD convertor using the following steps:
 - i. Draw the truth table for the 4 bit convertor (already given above)
 - ii. Draw the K map for each of the (four) outputs
 - iii. Calculate the logic equation for each output
 - iv. Draw the circuit on paper
 - v. Verify the circuit using the Circuitverse simulator. (Lab instructor will guide you on how to create an account use the simulator).
- b) Upload the write-up with the solved design problems given in write-up.


Observations and Results: Simulate as per instructions in Lab session. Take snapshots of the results and paste them in the write-ups.

Outcomes:

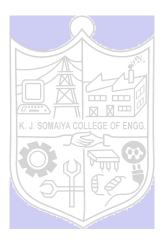

| Inpa | 15 | Outpats | |
|-----------|---|----------------|---|
| · ABC | | B4 B3 D2 B1 B0 | |
| 0000 | 0 | 0 0 0 0 0 | |
| | 1 | 0 0 0 0 1 | |
| 2001 | 0 | 0 0 0 10 | |
| 3001 | 1 | 000011 | |
| , | 0 | 000100 | |
| 50101 | | 000101 | |
| 60110 | | 000110 | |
| 70111 | 10,010 | 00111 | |
| 8 1 0 0 0 | | 01000 | |
| | 100 40 11 | 01001 | |
| h 1 0 1 1 | 19101 | 10000 | |
| 12 1 100 | 1 1101 | 10001 | |
| 2- | 1101 | 10010 | |
| 4 1 1 1 0 | CONTRACTOR OF THE PARTY OF THE | 10000 | |
| 5 1 1 1 1 | | 10101 | - |
| | | | |
| K Map for | r Bo | | |
| AB 00 00 | . 01 . 14 | 10 | |
| 00 00 | 1 , 31 | 3 0 2 Bo= D | |
| 01 0 + | | 7 0 - 6 | |
| 11 0 2 | 1 13 1 13 | 14 | |
| 10 0 8 | 1 9 11 | 0 14 | |
| | - | | |
| | | | |

| t N | lap for RI |
|----------|--|
| | $\begin{array}{cccccccccccccccccccccccccccccccccccc$ |
| | |
| | 4 0 5 7 7 7 6 |
| | 8 09 01 010 |
| X M | up for B2. |
| 40 00 | 0,01,10,10 |
| 00 0 | 0 0 1 0 3 ° 2 BZ= BC+AB |
| | + 1 5 1 7 1 6 |
| | 2 0 n · 1 13 1 m |
| 1010 | 8 0 1 0 0 10 |
| 200 | |
| 48 00 | p for B3 |
| 00 00 | M 1- |
| 01 04 | 0 5 0 7 0 6 |
| 11 12 | 15 0 19 |
| 00 18 | 1 2 0 10 0 10 |
| | 2 = (8) = x |
| kn. | p for By |
| 10 cm 00 | 01 11 16 100 100 |
| 00 | $B_{4} = A(+AB)$ |
| 01 | |
| 11 1 | In In I was a second to |
| 10 8 | 1 Lulla and Was Constant |
| | A 3 |
| | () [Sat + ga(t-2a) |
| | |

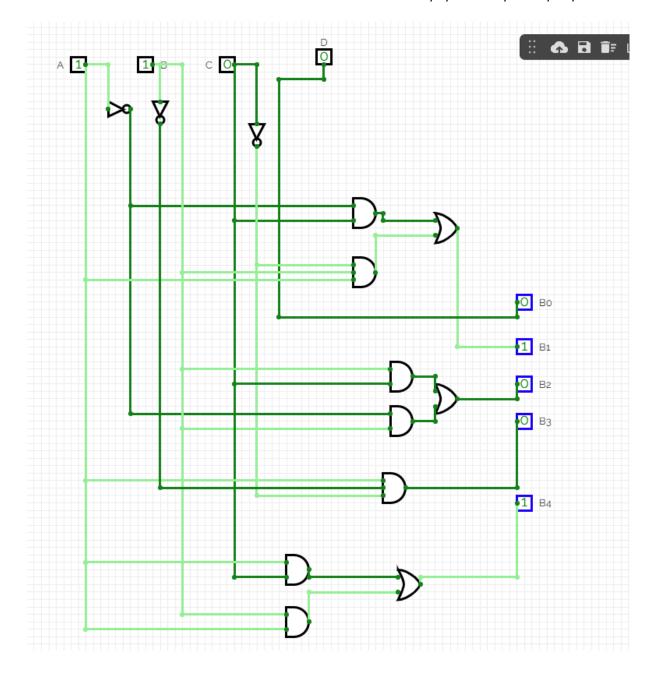

Conclusion: We constructed a binary to BCD convertor using basic logic gates such as AND OR NOT. We got the equation required using kmap method

Grade: AA / AB / BB / BC / CC / CD /DD

Signature of faculty in-charge with date

References:

Books/ Journals/ Websites:

1. R. P. Jain, "Modern Digital Electronics", Tata McGraw Hill.

