

ELCT201: DIGITAL LOGIC DESIGN

Prof. Dr. Eng. Tallal El-Shabrawy,
tallal.el-shabrawy@guc.edu.eg

Dr. Eng. Wassim Alexan,
wassim.joseph@guc.edu.eg

Lecture 6

محرم 1441 هـ
Spring 2020



Following the slides of Dr. Ahmed H. Madian

COURSE OUTLINE


1. Introduction
2. Gate-Level Minimization
3. Combinational Logic
4. Synchronous Sequential Logic
5. Registers and Counters
6. Memories and Programmable Logic

LECTURE OUTLINE

- Combinational Logic Circuits
 - Decoders
 - Encoders
 - Multiplexers
 - Tri-state Buffers

DECODERS

 - A Decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines
- If the n –bit coded information has unused combinations, the decoder may have fewer than 2^n outputs
- Consider a vending machine that takes 3 bits as input and releases a single product, out of the available 8 product sorts




DECODERS

- It is required to design a combinational circuit with two inputs (a, b) and four outputs (D_0, D_1, D_2, D_3) , such that:
 - $D_0 = 1$ when $a = 0$ and $b = 0$
 - $D_1 = 1$ when $a = 0$ and $b = 1$
 - $D_2 = 1$ when $a = 1$ and $b = 0$
 - $D_3 = 1$ when $a = 1$ and $b = 1$

DECODERS

Solution

 1. From the specifications of the circuit, determine the required number of inputs and outputs and assign a letter (symbol) to each



DECODERS

2. Derive the truth table that defines the required relationship between the inputs and outputs

Inputs		Outputs			
a	b	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

DECODERS

3. Obtain the simplified Boolean functions for each output as a function of the input variables


$$D_0 = a'b'$$

$$D_1 = a'b$$

$$D_2 = ab'$$


$$D_3 = ab$$

4. Sketch the logic diagram

 

3×8 DECODER

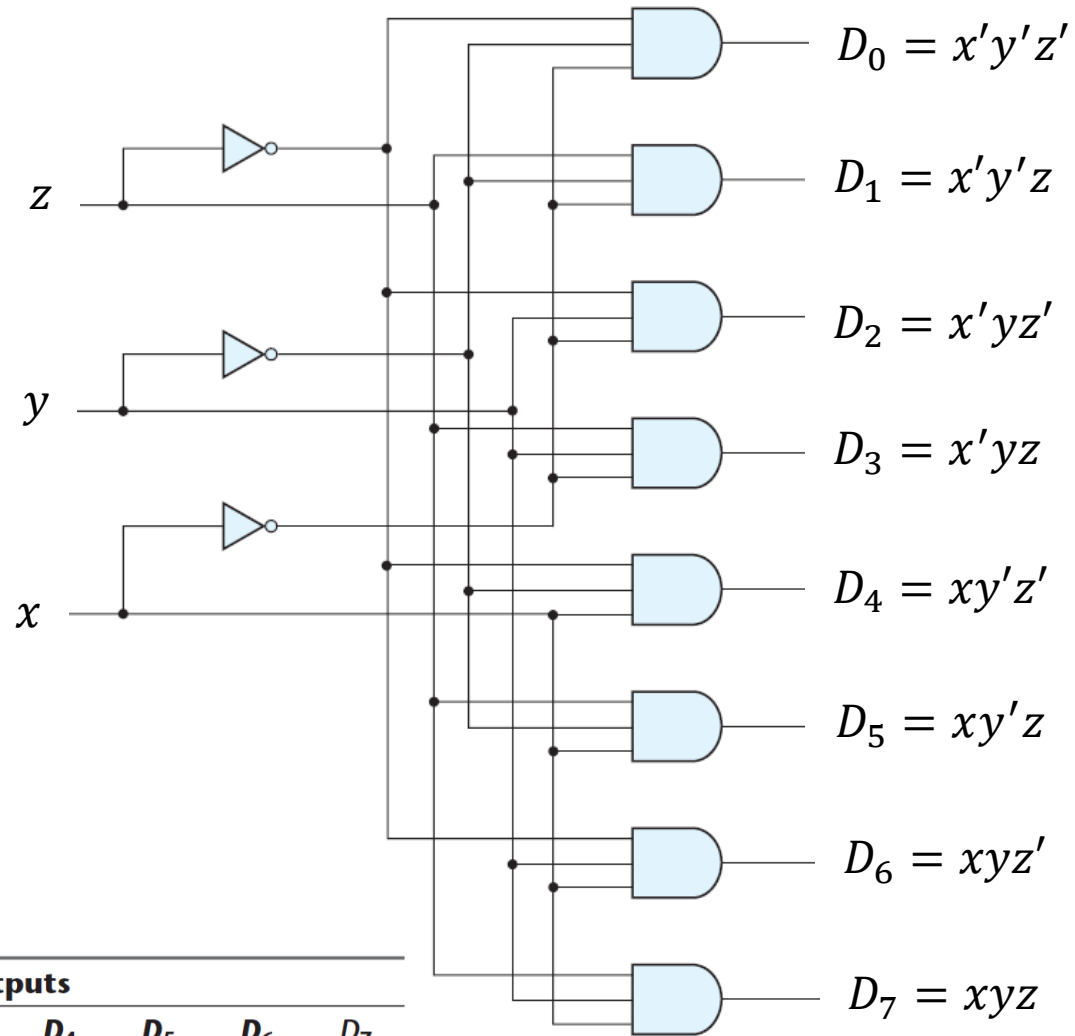- A 3×8 line decoder decodes 3 input bits into one of 8 possible outputs
- Each output represents one of the minterms of the 3 input variables




Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

2×4 DECODER

- A decoder could include an *Enable* input to control the circuit operation
- A decoder could be implemented with NAND gates and thus produces the minterms in their complemented form

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

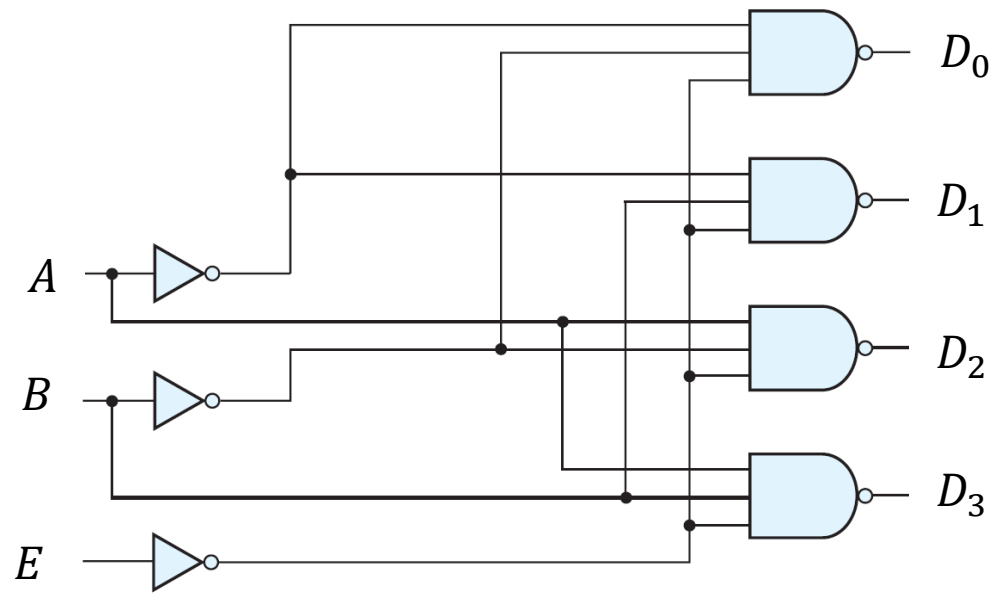

IMPLEMENTING FUNCTIONS USING DECODERS


- Any combinational circuit can be constructed using decoders and OR gates (the decoder generates the minterms and the OR gate performs the summation)
- **Example:** Implement a full adder circuit with a decoder and two OR gates
- Full adder equations:

$$S(x, y, z) = \Sigma m(1, 2, 4, 7) \text{ and}$$
$$C(x, y, z) = \Sigma m(3, 5, 6, 7)$$

- Since there are 3 inputs, we need a 3×8 decoder

IMPLEMENTING FUNCTIONS USING DECODERS

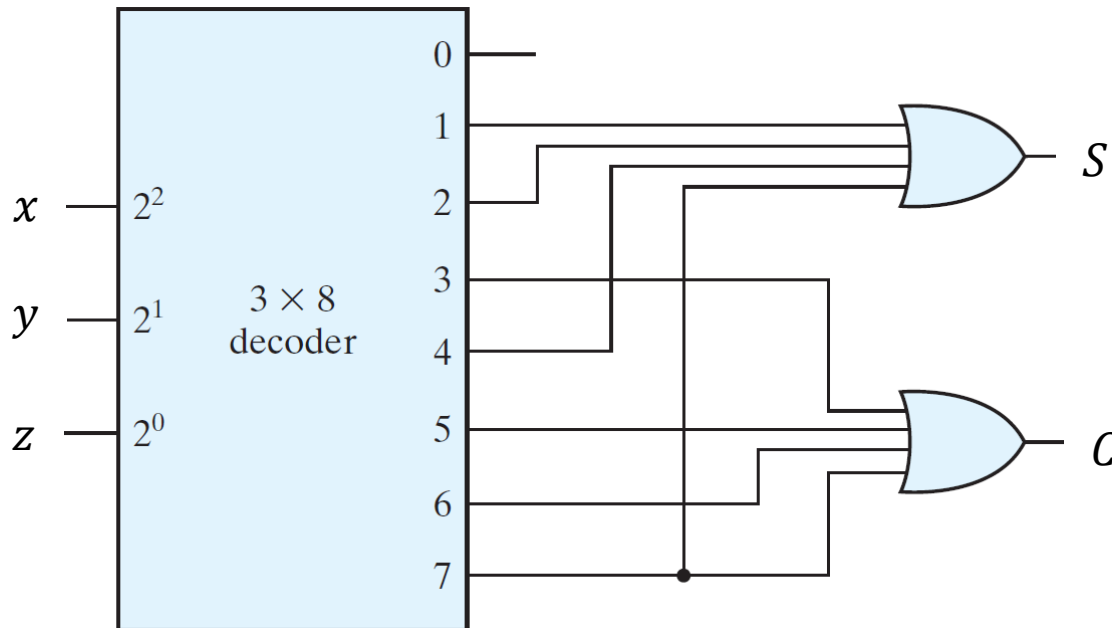
- $S(x, y, z) = \Sigma m(1, 2, 4, 7)$ and
- $C(x, y, z) = \Sigma m(3, 5, 6, 7)$



Inputs			Outputs	
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

DECODER EXPANSIONS

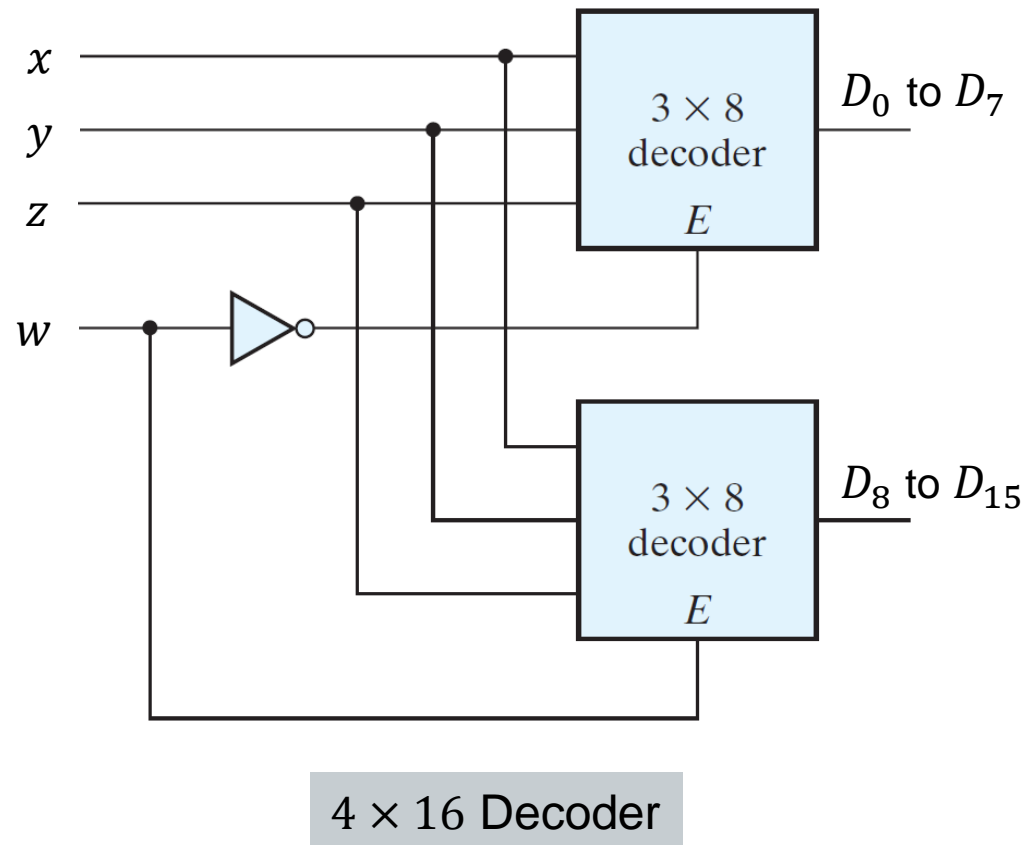
- Larger decoders can be constructed using a number of smaller ones
- For example, a 3×8 decoder can be built using a couple of 2×4 decoders and a 4×16 decoder can be built using a couple of 3×8 decoders



EXERCISE

- Can you sketch a 4×16 decoder using a number of 2×4 decoders?
- I am now giving you 5 minutes to attempt it
- After these 5 minutes, the lecture will continue

4 × 16 DECODER USING 2 × 4 DECODERS

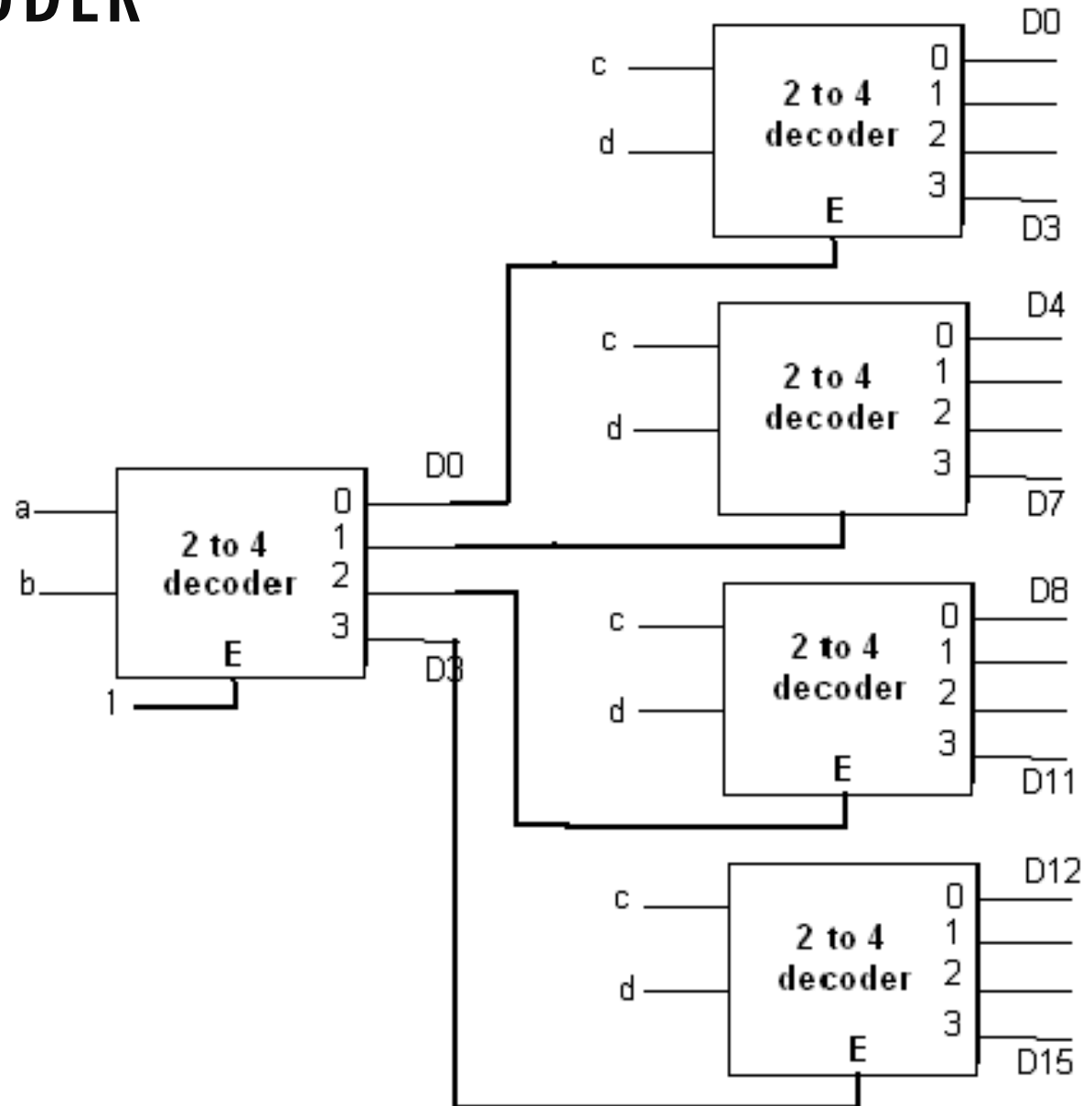

ENCODERS

- An encoder is a digital circuit that performs the inverse operation of a decoder
- An encoder has 2^n input lines and n output lines
- The output lines generate the binary equivalent of the input line whose value is 1

8×3 OCTAL-TO-BINARY ENCODER

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

*What happens if more than one input is active (set to HIGH) at the same time?
For example, D_3 and D_6 ?*

What happens if all inputs are equal to 0?

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

8×3 OCTAL-TO-BINARY ENCODER

What happens if more than one input is active (set to HIGH) at the same time? For example, D_3 and D_6 ?

- If D_3 and D_6 are active simultaneously, the output would be $(111)_2 = (7)_{10}$, because all three outputs would be equal to 1
- But this does not reflect the actual input which should have resulted in an output of $(011)_2 = (3)_{10}$ for D_3 or $(110)_2 = (6)_{10}$ for D_6
- To overcome this problem, we use *priority encoders*
- If we establish a higher priority for inputs with higher subscript numbers, and if both D_3 and D_6 are active at the same time, the output would be $(110)_2$ because D_6 has higher priority than D_3

$$x = D_4 + D_5 + D_6 + D_7$$


$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

8×3 OCTAL-TO-BINARY ENCODER

What happens if all inputs are equal to 0?

 - The encoder output would be $(000)_2$, but in fact this is the output when D_0 is equal to 1
- This problem can be solved by providing an extra output to indicate whether at least one input is equal to 1
- v is the valid output




4×2 PRIORITY ENCODER

- The input D_3 has the highest priority, regardless of the values of the other inputs
- Thus, if D_3 is 1, the output will indicate that $A_1A_0 = 11$, i.e. the code $A_1A_0 = 11$ means that any data appearing on line D_3 will have the highest priority and will pass through the system irrespective of other inputs
- If $D_2 = 1$ and $D_3 = 0$, the output code will be $A_1A_0 = 10$ and this means that D_2 has the highest priority in this case


Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

MAKING CONNECTIONS

 - Direct point-to-point connections between gates are made up of *wires*
- Routing one of many inputs to a single output is carried out using a *multiplexer*
- Routing a single input to one of many outputs is carried out using a *demultiplexer*



Multiplexer

 


Demultiplexer

MULTIPLEXERS

- A multiplexer is used to connect 2^n points to a single point
- The control signal pattern forms the binary index of the input to be connected to the output

A	Z
0	I_0
1	I_1




*Functional
form*

 



I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

*Logical
form*

MULTIPLEXERS

   


2×1 LINE MULTIPLEXER

  

4×1 LINE MULTIPLEXER

S_0	S_1	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


*Functional
form*

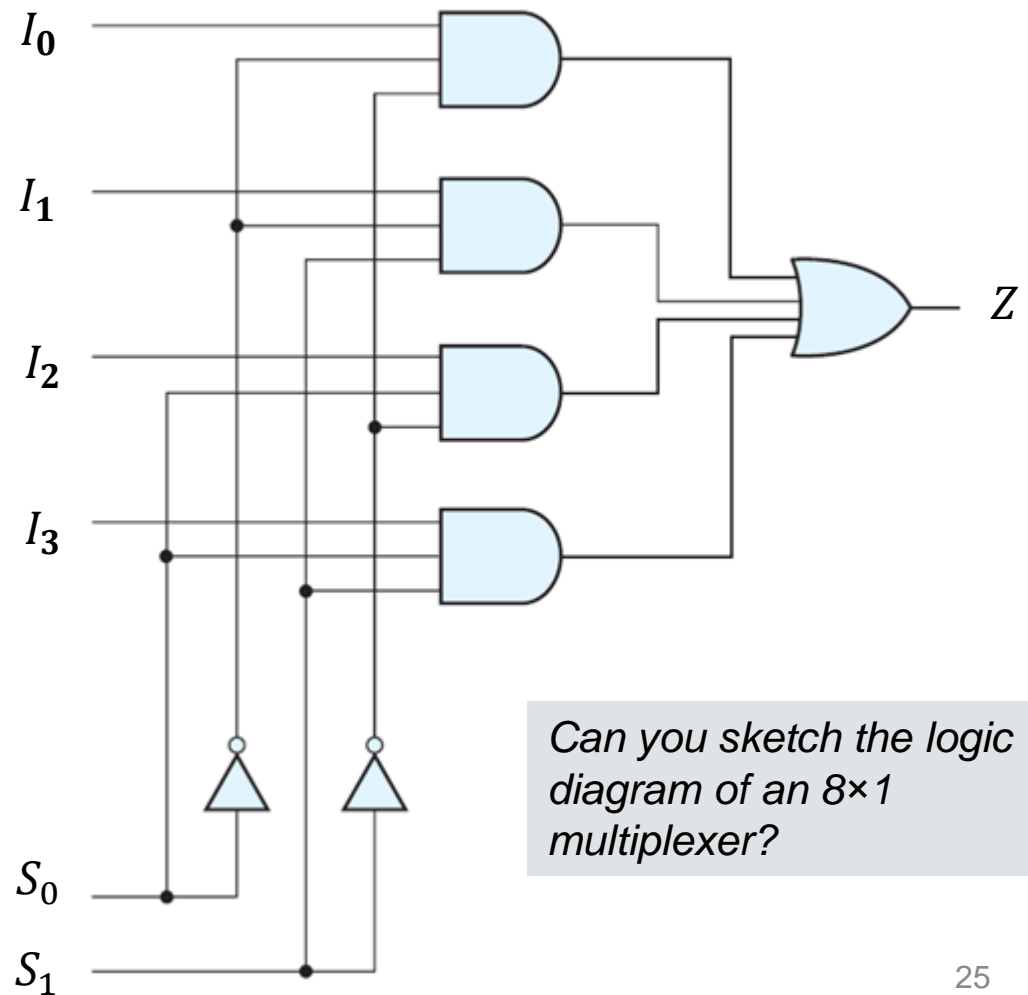

8×1 LINE MULTIPLEXER

- I am now giving you 5 minutes to attempt sketching the logic diagram of an 8×1 line multiplexer
- After these 5 minutes, the lecture will continue

8×1 LINE MULTIPLEXER

 


MULTIPLEXERS AS GENERAL-PURPOSE LOGIC

- A $2^{n-1}:1$ multiplexer can implement any function of n variables
- Steps:
 1. The Boolean function is listed in a truth table
 2. The first $n - 1$ variables in the table are applied to the selection inputs of the MUX
 3. For each combination of the selection variables, evaluate the output as a function of the last variable
 4. The values are then applied to the data inputs in the proper order

MULTIPLEXERS AS GENERAL-PURPOSE LOGIC: EXAMPLE I

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$


x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

 

MULTIPLEXERS AS GENERAL-PURPOSE LOGIC: EXAMPLE II


$$F(A, B, C, D) = \Sigma(1,3,4,11,12,13,14,15)$$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

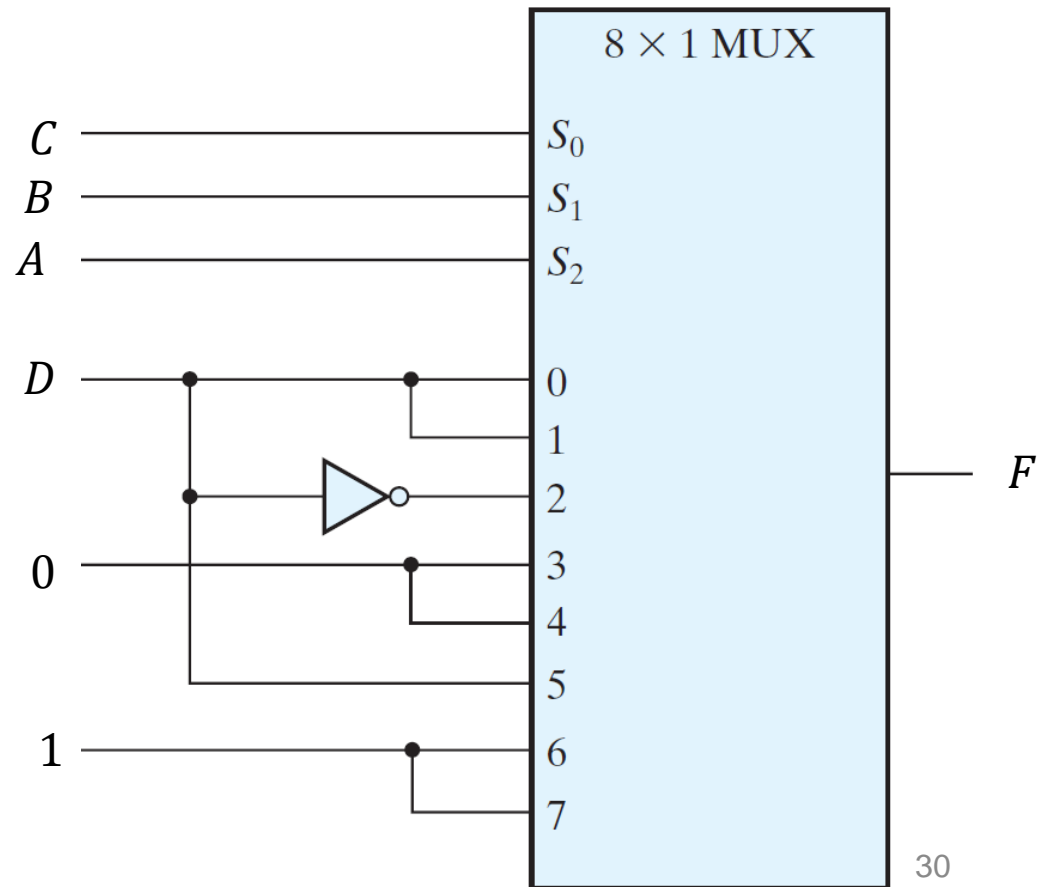


THREE-STATE BUFFERS (TRI-STATE BUFFERS)

 
- These are digital circuits that exhibit three states
- Two of these states are logic 0 and logic 1
- The third state is a *high-impedance* state in which:
 1. *The logic behaves like an open circuit*
 2. *The circuit has no logic significance*
 3. *The circuit connected to the output of the three-state gate is not affected by the inputs to the gate*



MULTIPLEXERS USING THREE-STATE BUFFERS

 

2 × 1 line MUX

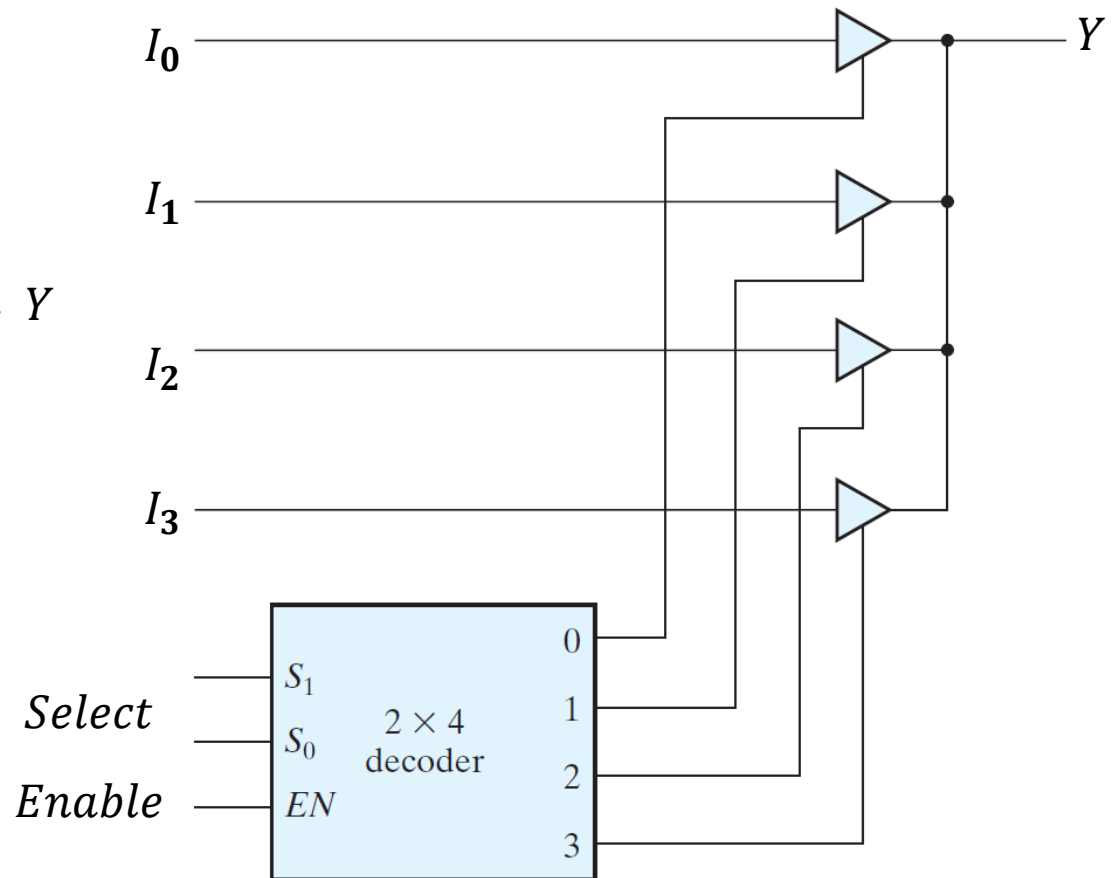

4 × 1 line MUX